

# BEEE Unit–5 Notes Basic Electronics Easy & Detailed Explanation for RGPV Students

## UNIT–5 TOPICS COVERED

### Digital Electronics

- Number Systems
- Number Conversion
- De Morgan's Theorem
- Logic Gates
- Half Adder
- Full Adder
- R-S Flip Flop
- J-K Flip Flop

### Semiconductor Electronics

- Semiconductors
- Diodes
- V-I Characteristics
- Bipolar Junction Transistor (BJT)
- CB, CE & CC Configurations
- Modes of Operation of BJT

## 1. NUMBER SYSTEMS

A number system is a method of representing numbers using digits or symbols.

### Types of Number Systems:

- Decimal Number System
- Binary Number System
- Octal Number System
- Hexadecimal Number System

### Decimal to Binary Conversion:

Repeatedly divide the number by 2 and write remainders.

### Binary to Decimal Conversion:

Multiply binary digits with powers of 2 and add them.

### Applications:

Computers, digital systems and electronic devices.

## 2. DE MORGAN'S THEOREM

First Theorem:

$$(A+B)' = A'B'$$

Second Theorem:

$$(AB)' = A'+B'$$

### Applications:

Logic circuit simplification and digital circuit design.

## 3. LOGIC GATES

Logic gates are electronic circuits used to perform logical operations.

### Types of Gates:

- AND Gate

- OR Gate
- NOT Gate
- NAND Gate
- NOR Gate
- XOR Gate

**Applications:**

Computers, calculators and digital systems.

#### 4. HALF ADDER

Half adder adds two binary digits.

Sum = A XOR B

Carry = AB

**Limitation:**

Cannot add carry input.

#### 5. FULL ADDER

Full adder adds three binary digits including carry input.

Sum = A XOR B XOR C

Carry = AB + BC + CA

**Applications:**

Computers and calculators.

#### 6. R-S FLIP FLOP

Basic memory element storing one bit.

Inputs:

- Set (S)
- Reset (R)

Applications:

Registers and memory circuits.

#### 7. J-K FLIP FLOP

Improved version of R-S flip flop.

Advantages:

- No invalid state
- Toggle operation possible

Applications:

Counters and registers.

#### 8. SEMICONDUCTORS

Semiconductors are materials having conductivity between conductors and insulators.

Examples:

- Silicon
- Germanium

Types:

- Intrinsic Semiconductor
- Extrinsic Semiconductor

## 9. DIODE

A diode allows current in one direction only.

### **Forward Bias:**

Current flows easily.

### **Reverse Bias:**

Very small current flows.

Applications:

Rectifiers and voltage regulators.

## 10. V-I CHARACTERISTICS OF DIODE

### **Forward Bias Region:**

Current increases rapidly after knee voltage.

### **Reverse Bias Region:**

Very small reverse current flows.

### **Breakdown Region:**

Large reverse current suddenly flows.

## 11. BIPOLAR JUNCTION TRANSISTOR (BJT)

A transistor is a three terminal semiconductor device used for amplification and switching.

Types:

- NPN Transistor
- PNP Transistor

Terminals:

- Emitter
- Base
- Collector

Applications:

Amplifiers and switching circuits.

## 12. TRANSISTOR CONFIGURATIONS

### **Common Base (CB):**

- Low input resistance
- High voltage gain

### **Common Emitter (CE):**

- High current gain
- High voltage gain

### **Common Collector (CC):**

- High input resistance
- Low output resistance

## 13. MODES OF OPERATION OF BJT

### **1. Active Region:**

Used for amplification.

### **2. Cutoff Region:**

Transistor OFF.

### **3. Saturation Region:**

Transistor fully ON.

### **MOST IMPORTANT 14 MARK QUESTIONS**

1. Explain number systems and conversions.
2. Explain De Morgan's theorem.
3. Explain logic gates with truth tables.
4. Explain half adder and full adder.
5. Explain R-S and J-K flip flop.
6. Explain semiconductors and types.
7. Explain diode and V-I characteristics.
8. Explain BJT and working principle.
9. Explain transistor configurations.
10. Explain modes of operation of BJT.

### **EXAM TIPS**

- Learn truth tables properly.
- Practice number conversions daily.
- Draw transistor diagrams neatly.
- Learn logic gate symbols.
- Practice Boolean simplification.